

## Conduction Cooled Capacitor Application Notes

Conduction cooled capacitors are designed for use in high power resonant (tank) circuits. Typically, these circuits consist of a capacitor and an inductor connected either in series or parallel.

The resonant frequency in these LC circuits is found when the reactance of the capacitor and the inductor are equal


$$X_L = X_C$$

$$\omega L = 1/\omega C$$


$$\omega = 1/\sqrt{LC}$$

$$f_0 = 1/(2\pi\sqrt{LC})$$

Series resonant

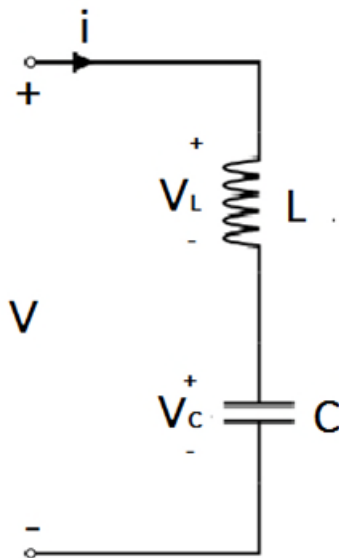

Parallel resonant

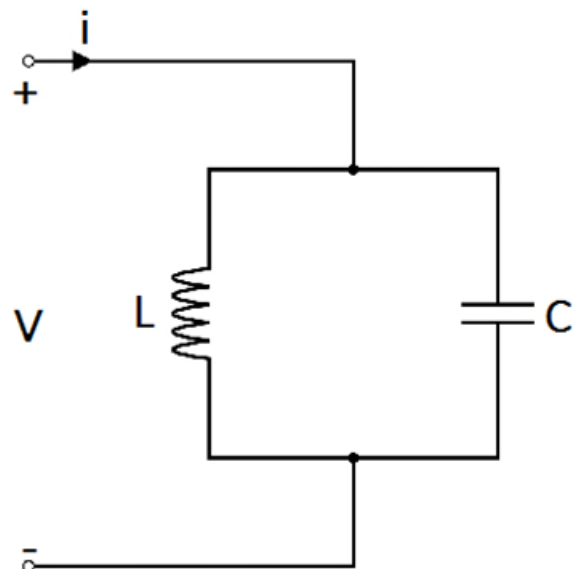


### Active, apparent and reactive power

Active or real power is the actual power that can be delivered to the load.

$$P = V * I \text{ Watts}$$

Reactive or imaginary power is

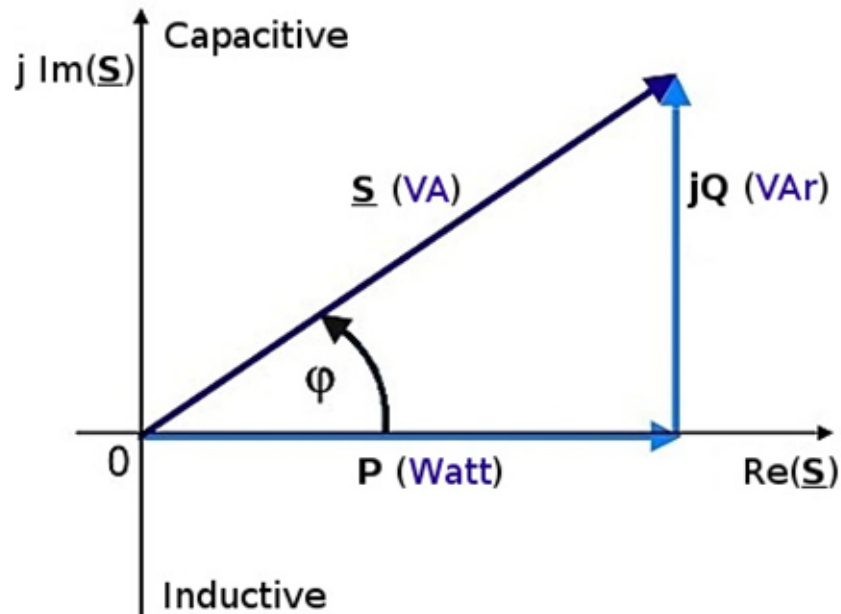

$$\text{Reactive power} = V \cdot I \cdot \sin \Phi = V^2 \cdot 2 \cdot \pi \cdot f \cdot C$$

Reactive power is expressed in volt ampere reactive (var).

Apparent power is the power supplied to the circuit. Apparent power is measured in volt-amperes (VA). Apparent power is the voltage multiplied by the current in an AC system. Apparent power is the vector sum of the active and reactive power.

$$S = \sqrt{(Q^2 + P^2)}$$

S= apparent power (Kilovolt amps, kva)

Q= reactive power (kilovolt amp reactive, kvar)

P= active power (kilowatts, kw)